



# Circuits

- Elements are connected by wires.
- Any connected region of wire has the same potential.
- The potential difference across an element is the *element's* “voltage.”

