

Capacitors in Parallel

- Both ends connected together by wire
- Same voltage: $V_1 = V_2 = V_{eq}$
- Share Charge: $Q_{eq} = Q_1 + Q_2$
- Equivalent C: $C_{eq} = C_1 + C_2$

Add areas – remember $C = \epsilon_0 A/d$

