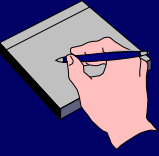


Example



Parallel Practice

A $4 \mu\text{F}$ capacitor and $6 \mu\text{F}$ capacitor are connected in parallel and charged to 5 volts. Calculate C_{eq} , and the charge on each capacitor.

$$C_{\text{eq}} = C_4 + C_6 = 4 \mu\text{F} + 6 \mu\text{F} = 10 \mu\text{F}$$

$$Q_4 = C_4 V_4 = (4 \mu\text{F})(5 \text{ V}) = 20 \mu\text{C}$$

$$Q_6 = C_6 V_6 = (6 \mu\text{F})(5 \text{ V}) = 30 \mu\text{C}$$

$$Q_{\text{eq}} = C_{\text{eq}} V_{\text{eq}} = (10 \mu\text{F})(5 \text{ V}) = 50 \mu\text{C} = Q_4 + Q_6$$

