

Comparison: *Series vs. Parallel*

Series

- Can follow a wire from one element to the other with no branches in between.

Parallel

- Can find a loop of wire containing both elements but no others (may have branches).

