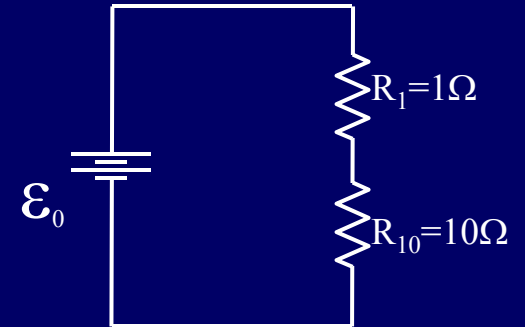




# ACT: Series Circuit

Compare  $V_1$  the voltage across  $R_1$ , with  $V_{10}$  the voltage across  $R_{10}$ .



1.  $V_1 > V_{10}$

2.  $V_1 = V_{10}$

3.  $V_1 < V_{10}$