

Resistors in Parallel

- **Two wires:**
 - Effectively adding the Area
 - Since $R \propto 1/A$ add $1/R$:

$$1/R_{\text{eq}} = 1/R_1 + 1/R_2$$

