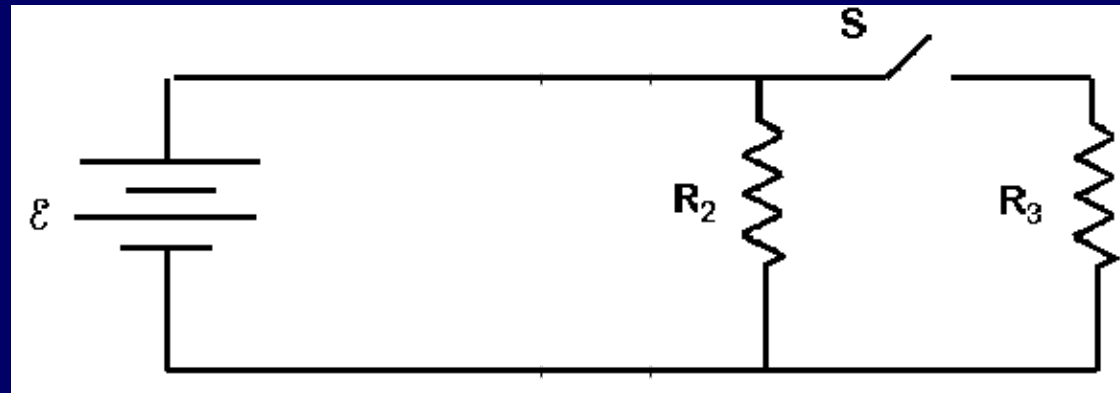


Preflight 5.5

What happens to the current through R_2 when the switch is closed?

- Increases
- Remains Same
- Decreases



ACT: Parallel Circuit

What happens to the current through the battery?

- (1) Increases
- (2) Remains Same
- (3) Decreases

