

# Example



## Simple Circuit

- Visualization
- Practice...

- Calculate I when  $\varepsilon=24$  Volts and  $R = 8 \Omega$
- Ohm's Law:  $V = IR$

$$I = V/R = 3 \text{ Amps}$$

