

# Resistors in Series

- One wire:
  - Effectively adding lengths:
    - $R_{eq} = \rho(L_1 + L_2)/A$
  - Since  $R \propto L$  add resistance:

$$R_{eq} = R_1 + R_2$$

