

Preflight 5.3

Compare I_1 the current through R_1 , with I_{10} the current through R_{10} .

1. $I_1 < I_{10}$
2. $I_1 = I_{10}$
3. $I_1 > I_{10}$

