

Preflight 6.2

Calculate the current through resistor 2.

- 1) $I_2 = 0.5 \text{ A}$
- 2) $I_2 = 1.0 \text{ A}$
- 3) $I_2 = 1.5 \text{ A}$

$$\mathcal{E}_1 - \mathcal{E}_2 - I_2 R = 0$$

$$\Rightarrow I_2 = 0.5 \text{ A}$$

