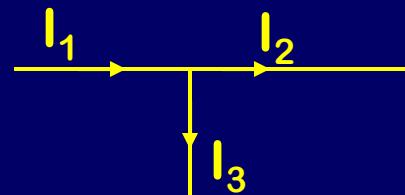


# Kirchhoff's Junction Rule

**Current Entering = Current Leaving**

$$I_1 = I_2 + I_3$$



## Preflight 6.3

Calculate the current through battery.

- 1)  $I_B = 0.5 \text{ A}$
- 2)  $I_B = 1.0 \text{ A}$
- 3)  $I_B = 1.5 \text{ A}$

$$I_B = I_1 + I_2 = 1.5 \text{ A}$$

