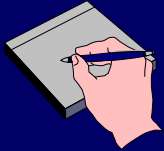


Example



You try it!

In the circuit below you are given \mathcal{E}_1 , \mathcal{E}_2 , R_1 , R_2 and R_3 . Find I_1 , I_2 and I_3 .

