
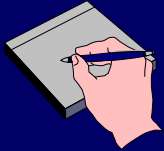


Example

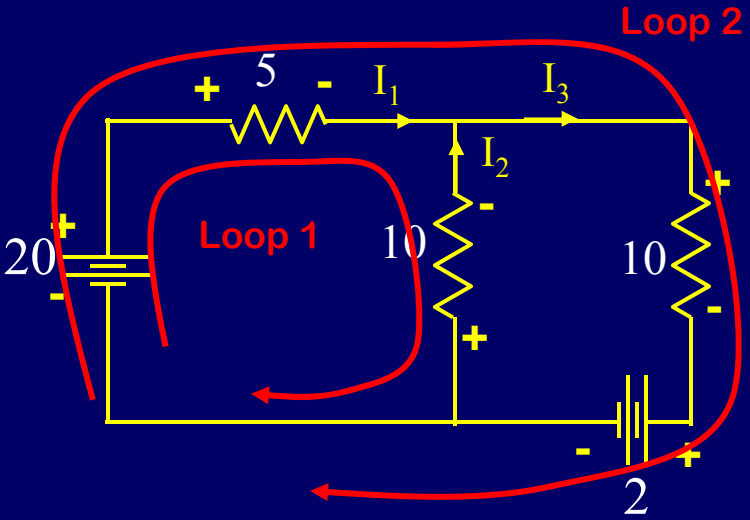

Let's put in real numbers

In the circuit below you are given \mathcal{E}_1 , \mathcal{E}_2 , R_1 , R_2 and R_3 . Find I_1 , I_2 and I_3 .



1. Loop 1: $20 - 5I_1 + 10I_2 = 0$
2. Loop 2: $20 - 5I_1 - 10I_3 - 2 = 0$
3. Junction: $I_3 = I_1 + I_2$

solution: substitute Eq.3 for I_3 in Eq. 2:

$$20 - 5I_1 - 10(I_1 + I_2) - 2 = 0$$

rearrange: $15I_1 + 10I_2 = 18$

rearrange Eq. 1: $5I_1 - 10I_2 = 20$

Now we have 2 eq., 2 unknowns. Continue on next slide