

Kirchhoff's Rules

- **Kirchhoff's Junction Rule (KJR):**
 - Current going in equals current coming out.
- **Kirchhoff's Loop Rule (KLR):**
 - Sum of voltage drops around a loop is zero.