

Kirchhoff's Junction Rule (KJR)

- Conceptual basis: **conservation of charge**
- At any junction in a circuit, the current that enters the junction equals the current that leaves the junction

- Example:

At junction:

$$I_1 + I_2 = I_3$$

