

Kirchhoff's Loop Rule (KLR)

- Conceptual basis: **conservation of energy**
- Going around any complete loop in a circuit, the sum total of all the potential differences is zero
- Example:

Around the right loop:

$$\varepsilon_2 + I_3 R_3 + I_2 R_2 = 0$$

