

Using Kirchhoff's Rules

(1) Label all currents

Choose any direction

(2) Label $+$ / $-$ for all elements

Current goes $+\Rightarrow-$ (for resistors)

(3) Choose loop and direction

(4) Write down voltage drops

Be careful about signs

