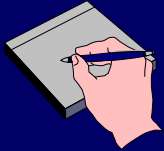



Example



Loop Rule Practice

Find I:

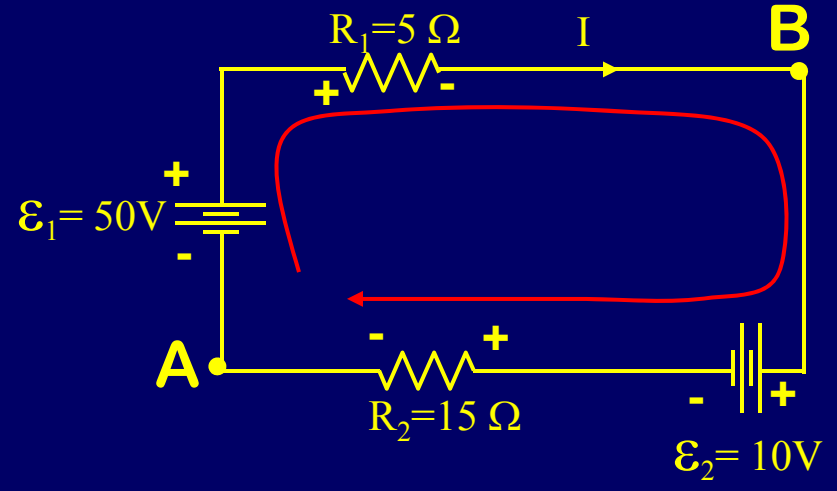- Label currents
- Label elements +/-
- Choose loop
- Write KLR



$$+\epsilon_1 - IR_1 - \epsilon_2 - IR_2 = 0$$
$$+50 - 5I - 10 - 15I = 0$$
$$I = +2 \text{ Amps}$$