



# ACT: KLR

Resistors  $R_1$  and  $R_2$  are

- 1) in parallel    2) in series    3) neither

