

Physics 102: Lecture 7

RC Circuits