

Recall

- First we covered circuits with batteries and capacitors
 - series, parallel
- Then we covered circuits with batteries and resistors
 - series, parallel
 - Kirchhoff's Loop and Junction Relations
- Today: circuits with batteries, resistors, and capacitors