

# Discharging Capacitors

- Capacitor is initially charged ( $Q$ ) and switch is open. Switch is then closed. What is current  $I_0$  in circuit immediately thereafter?
- What is current  $I_\infty$  in circuit a long time later?

