

# Discharging Capacitors


- Capacitor is initially charged ( $Q$ ) and switch is open. Switch is then closed. What is current  $I_0$  in circuit immediately thereafter?

- KLR:  $Q/C - I_0 R = 0$

- So,  $I_0 = Q/RC$

- What is current  $I_\infty$  in circuit a long time later?

- $I_\infty = 0$

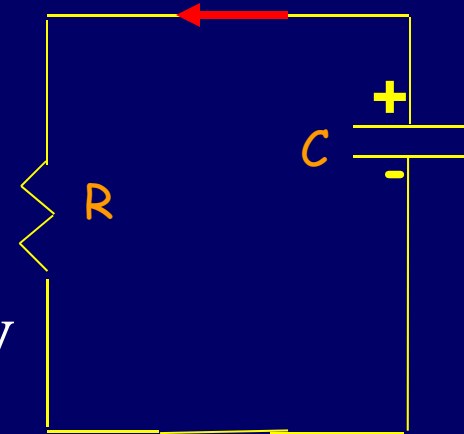

Demo