



ACT: RC Circuits

Both switches are closed. What is the final charge on the capacitor after the switches have been closed a long time?

1) $Q = 0$

2) $Q = C \mathcal{E} / 3$

3) $Q = C \mathcal{E} / 2$

4) $Q = C \mathcal{E}$

