

What is the time constant?



- The time constant $\tau = RC$.
- Given a capacitor starting with no charge, the **time constant** is the amount of time an RC circuit takes to charge a capacitor to about **63.2%** of its final value.
- The **time constant** is the amount of time an RC circuit takes to discharge a capacitor by about **63.2%** of its original value.