

# Example

## Time Constant Demo

Each circuit has a 1 F capacitor charged to 100 Volts.  
When the switch is closed:

- Which system will be brightest?
- Which lights will stay on longest?
- Which lights consumes more energy?

