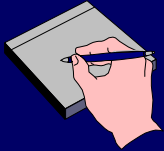


Example

Practice!



Calculate current immediately after switch is closed:


$$\mathcal{E} - I_0 R - q_0 / C = 0$$

$$\mathcal{E} - I_0 R - 0 = 0$$

$$I_0 = \mathcal{E} / R$$

Calculate current after switch has been closed for 0.5 seconds:
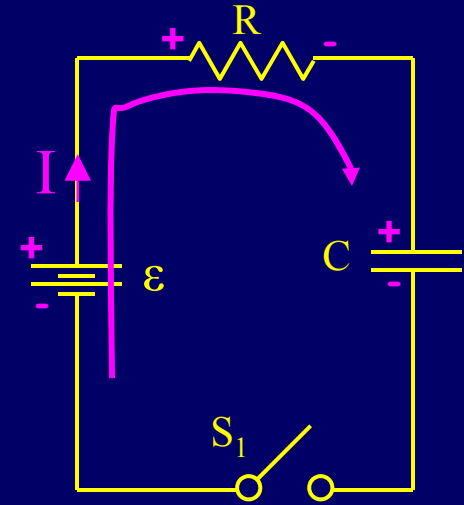
$$I = I_0 e^{\frac{-t}{RC}} = \frac{\mathcal{E}}{R} e^{\frac{-0.5}{RC}} = \frac{20}{10} e^{\frac{-0.5}{10 \times 0.03}} = \frac{20}{10} e^{\frac{-0.5}{10 \times 0.03}} = 0.38 \text{ Amps}$$



$R = 10 \Omega$
 $C = 30 \text{ mF}$
 $\mathcal{E} = 20 \text{ Volts}$

Calculate current after switch has been closed for a long time:

After a long time current through capacitor is zero!

Calculate charge on capacitor after switch has been closed for a long time:

$$\mathcal{E} - IR - q_\infty / C = 0$$

$$\mathcal{E} - 0 - q_\infty / C = 0$$

$$q_\infty = \mathcal{E} C$$