



# RC Summary

## Charging

$$q(t) = q_{\infty}(1 - e^{-t/RC})$$

$$V(t) = V_{\infty}(1 - e^{-t/RC})$$

$$I(t) = I_0 e^{-t/RC}$$

## Discharging

$$q(t) = q_0 e^{-t/RC}$$

$$V(t) = V_0 e^{-t/RC}$$

$$I(t) = I_0 e^{-t/RC}$$

## Time Constant $\tau = RC$

Large  $\tau$  means long time to charge/discharge

**Short term:** Charge doesn't change (often zero or max)

**Long term:** Current through capacitor is zero.