
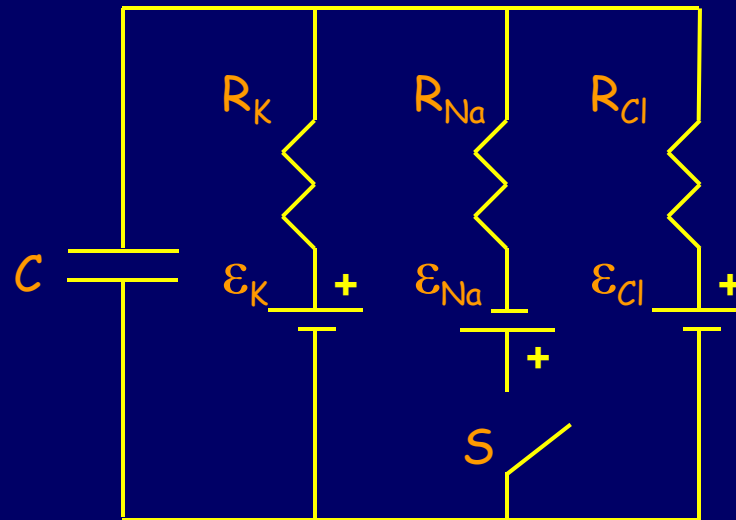


RC Circuits

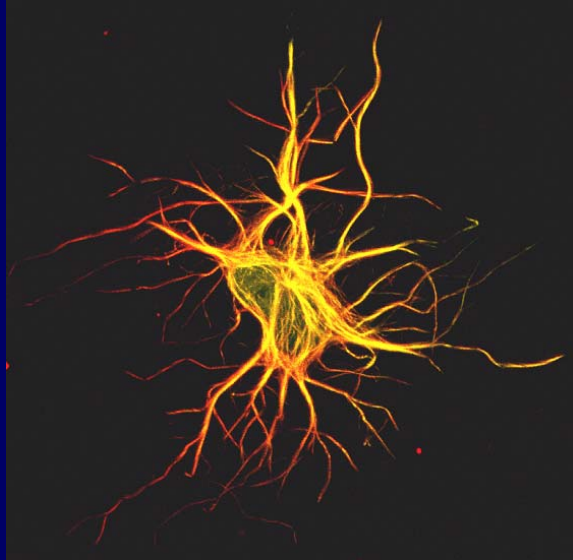- Circuits that have both resistors and capacitors:



- With **resistance** in the circuits, **capacitors** do not **charge** and **discharge** instantaneously – it takes time (even if only fractions of a second).