

Charging Capacitors

- Capacitor is initially uncharged and switch is open. Switch is then closed. What is current I_0 in circuit immediately thereafter?
- What is current I_∞ in circuit a long time later?

