

Preflight 11.6

The **good news** is you are going on a trip to France. The **bad news** is that in France the outlets have 240 volts. You remember from P102 that you need a transformer, so you wrap 100 turns around the primary. How many turns should you wrap around the secondary if you need 120 volts out to run your hair dryer?

1) 50

2) 100

3) 200

$$\frac{V_s}{V_p} = \frac{N_s}{N_p}$$

