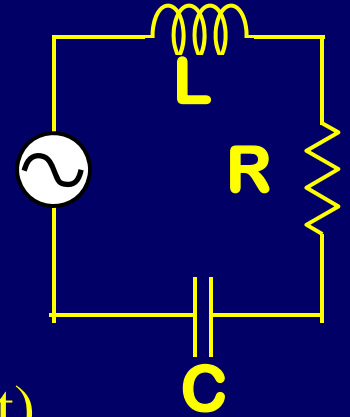




ACT: AC Circuit Voltages



An AC circuit with $R = 2 \Omega$, $C = 15 \text{ mF}$, and $L = 30 \text{ mH}$ has a current $I(t) = 0.5 \sin(8\pi t)$ amps. Calculate the maximum voltage across R , C , and L .



Now the frequency is increased so $I(t) = 0.5 \sin(16\pi t)$. Which element's maximum voltage decreases?

- 1) $V_{R,\max}$
- 2) $V_{C,\max}$
- 3) $V_{L,\max}$