Resonance



R is independent of f


 X_L increases with f

 $X_L = 2\pi f L$

- X_{c} decreases with f $X_{C} = 1/(2\pi fC)$
- **Z:** X_L and X_C subtract

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

Resonance in AC Circuits

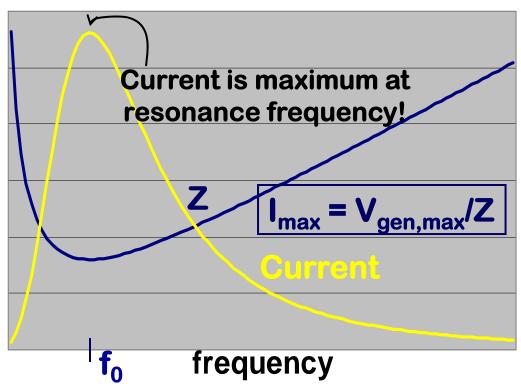

Resonance:
$$X_L = X_C$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$