
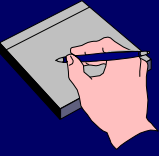


# Phasor Diagrams

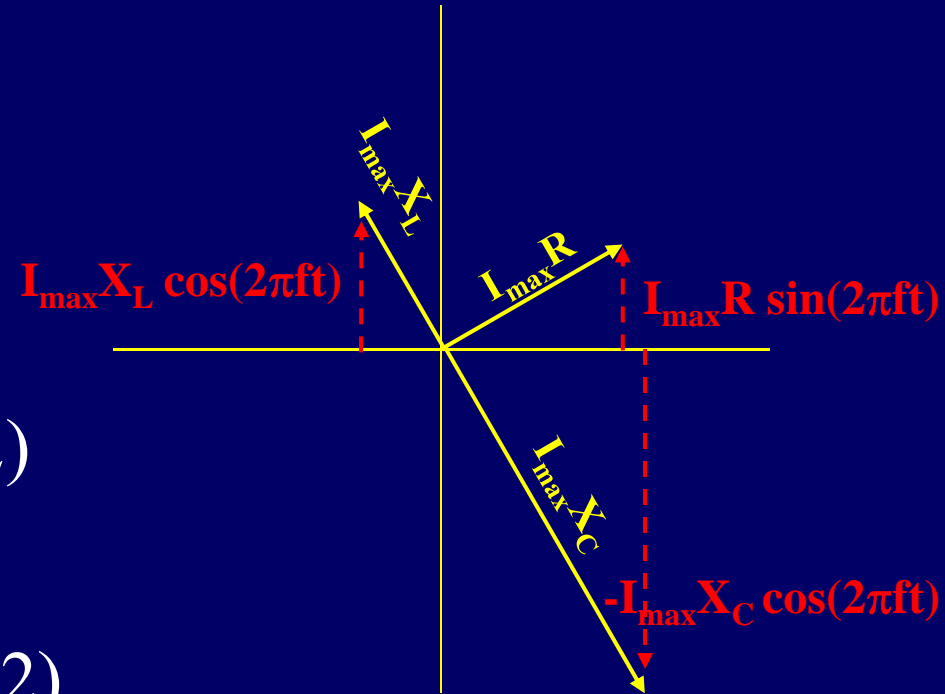

## Instantaneous Values:

- $I = I_{\max} \sin(2\pi ft)$
- $V_R = I_{\max} R \sin(2\pi ft)$
- $V_C = I_{\max} X_C \sin(2\pi ft - \pi/2)$   
 $= -I_{\max} X_C \cos(2\pi ft)$
- $V_L = I_{\max} X_L \sin(2\pi ft + \pi/2)$   
 $= I_{\max} X_L \cos(2\pi ft)$



**Voltage across resistor is always in phase with current!**

**Voltage across capacitor always lags current!**

**Voltage across inductor always leads current!**