



Kirchhoff: generator voltage

- Instantaneous voltage across generator (V_{gen}) must equal sum of voltage across all of the elements at all times:


$$V_{\text{gen}}(t) = V_R(t) + V_C(t) + V_L(t)$$

$$V_{\text{gen,max}} = \sqrt{V_{R,\text{max}}^2 + (V_{L,\text{max}} - V_{C,\text{max}})^2}$$

$$\tan \phi = \frac{V_{L,\text{max}} - V_{C,\text{max}}}{V_{R,\text{max}}}$$

“phase angle”

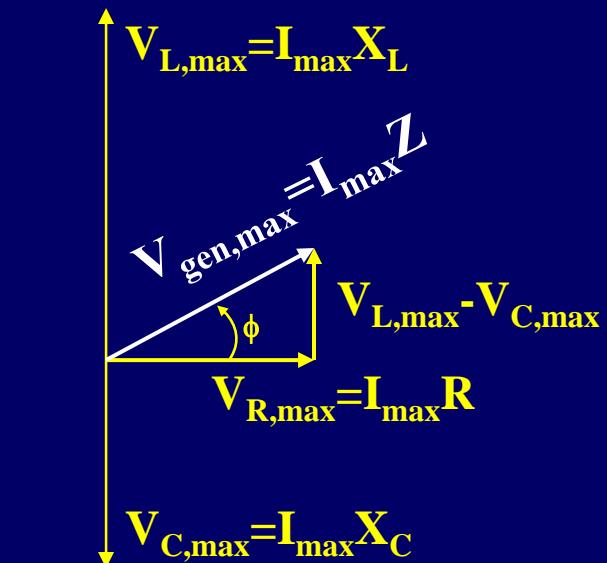Define impedance Z : $V_{\text{gen,max}} \equiv I_{\text{max}} Z$



$$Z = \sqrt{R^2 + (X_L - X_C)^2} \quad \tan(\phi) = \frac{(X_L - X_C)}{R}$$

“**Impedance Triangle**”