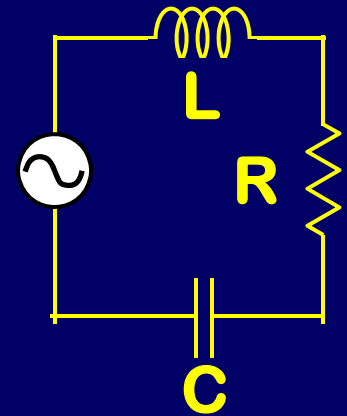


Preflight 14.1



As the frequency of the circuit is either raised above or lowered below the resonant frequency, the impedance of the circuit:

Always increases

Only increases for lowering the frequency

Only increases for raising the frequency

