Preflight 14.3

At the resonant frequency, which of the following is true?

- I leads V_{generator}
- I lags V_{generator}
- I is in phase with V_{generator}

