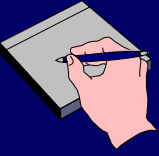


What is it good for?



- Current through circuit depends on frequency (maximum at resonance frequency f_0)
 - Radio receiver
 - Stereo equalizer
 - NMR/MRI

