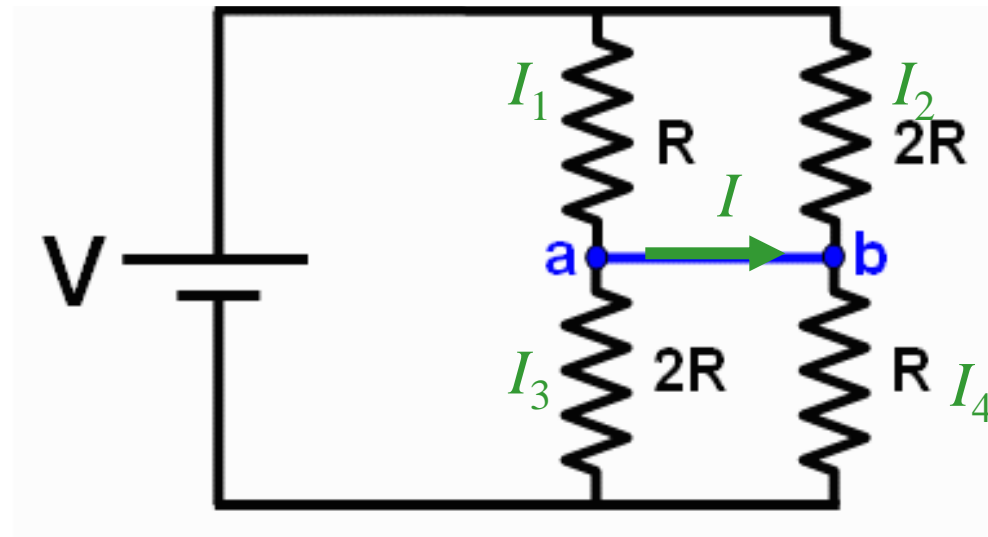
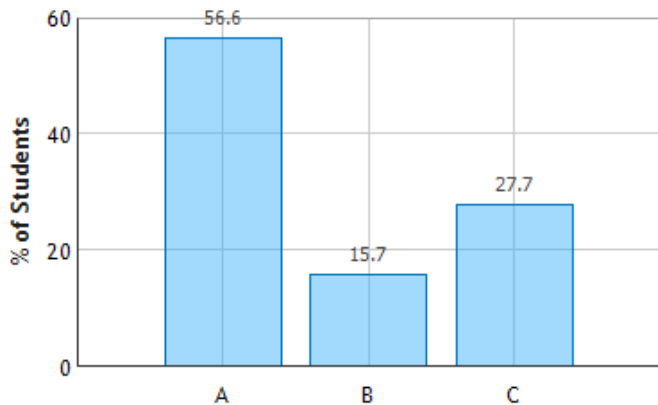


# CheckPoint 3a

Consider the circuit shown below. Note that this question is *not* identical to the similar looking one you answered in the prelecture.



Which of the following best describes the current flowing in the blue wire connecting points **a** and **b**?

- A. Positive current flows from a to b**
- C. No current flows between a and b**

- B. Positive current flows from b to a**

$$I_1 R - I_2 (2R) = 0 \quad \rightarrow \quad I_2 = \frac{1}{2} I_1$$

$$I_4 R - I_3 (2R) = 0 \quad \rightarrow \quad I_4 = 2 I_3$$

$$I = I_1 - I_3$$

$$I + I_2 = I_4 \quad \rightarrow \quad I_1 - I_3 + \frac{1}{2} I_1 = 2 I_3 \quad \rightarrow \quad I_1 = 2 I_3 \quad \rightarrow \quad I = +I_3$$