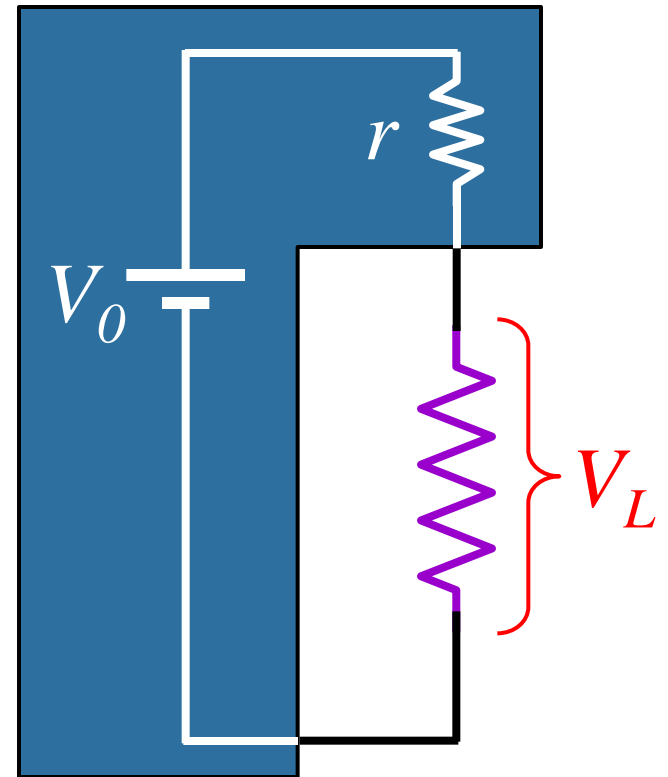
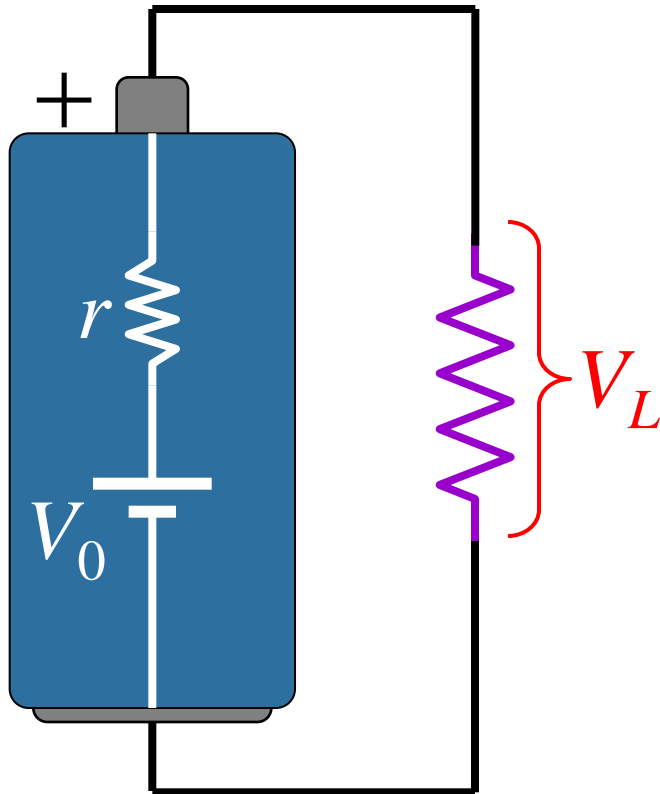


# Model for Real Battery: Internal Resistance



Usually can't supply too much current to the load  
without voltage "sagging"