

# Kirchhoff's Current Rule

$$\sum I_{in} = \sum I_{out}$$

Kirchhoff's Current Rule states that the sum of all currents entering any given point in a circuit must equal the sum of all currents leaving the same point.

**WHY?**

Electric Charge is Conserved