
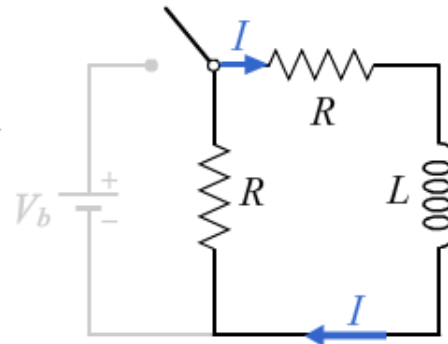


Time Constant  $\tau = \frac{L}{2R}$

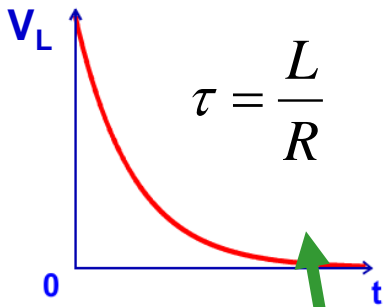


$$I(t) = \frac{V_b}{R} e^{-2Rt/L}$$


$$V_L(t) = -2V_b e^{-2Rt/L}$$



Lecture:

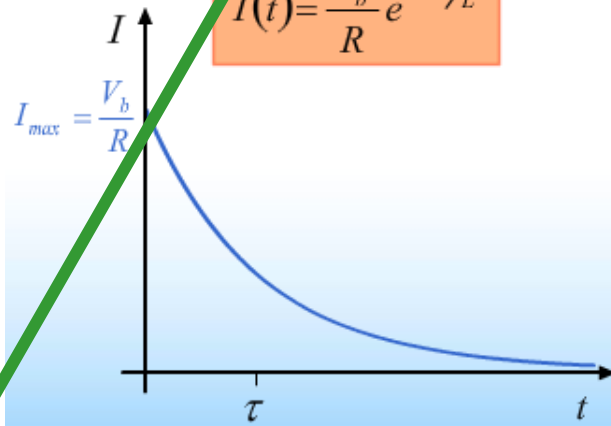

Prelecture:

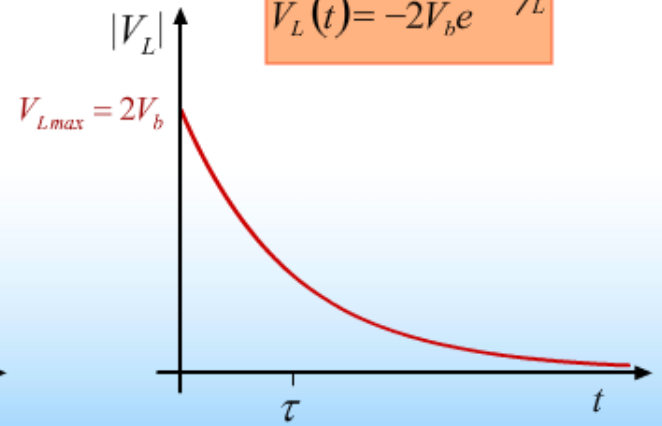

Did we mess up?

No: The resistance is simply twice as big in one case.