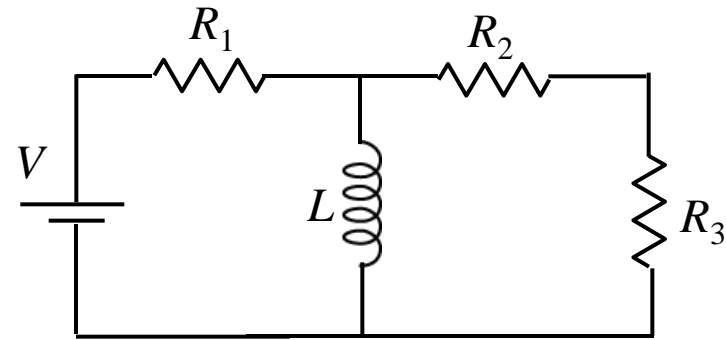


# Calculation



The switch in the circuit shown has been open for a long time. At  $t = 0$ , the switch is closed.

What is  $dI_L/dt$ , the time rate of change of the current through the inductor immediately after switch is closed



$$V_L(t = 0+) = V(R_2 + R_3)/(R_1 + R_2 + R_3)$$

A)  $\frac{dI_L}{dt} = \frac{V}{L} \frac{R_2 + R_3}{R_1}$

B)  $\frac{dI_L}{dt} = 0$

C)  $\frac{dI_L}{dt} = \frac{V}{L} \frac{R_2 + R_3}{R_1 + R_2 + R_3}$

D)  $\frac{dI_L}{dt} = \frac{V}{L}$

The time rate of change of current through the inductor  $(dI_L/dt) = V_L/L$

→  $\frac{dI_L}{dt} = \frac{V}{L} \frac{R_2 + R_3}{R_1 + R_2 + R_3}$