

# The Big Ideas L9-18

## Kirchoff's Rules

- Sum of voltages around a loop is zero
- Sum of currents into a node is zero
- Kirchoff's rules with capacitors and inductors
  - In RC and RL circuits: charge and current involve exponential functions with time constant: “charging and discharging”
  - E.g.  $IR + \frac{Q}{C} = V$
- Capacitors and inductors store energy

## Magnetic fields

- Generated by electric currents (no magnetic charges)
- Magnetic forces only on charges in motion  $\vec{F}_{mag} = q\vec{v} \times \vec{B}$
- Easiest to calculate with Ampere's Law  $\oint \vec{B} \cdot d\vec{\ell} = \mu_0 I_{enclosed}$
- Changing magnetic fields can generate electric fields! FARADAY'S LAW

$$\int \vec{E} \cdot d\vec{\ell} = EMF = \Delta V = -\frac{d}{dt} \int B \cdot dA = -\frac{d\phi_{mag}}{dt}$$