

Example: RL Circuit $X_c = 0$

