

Big Idea

KVR

$$L \frac{d^2 Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} - \mathcal{E}_m \sin(\omega t) = 0$$

Maximum Values (easy $V=IR$)

$$I_{max} = \mathcal{E}_{max} / Z$$

$$V_{Rmax} = I_{max} R$$

$$V_{Lmax} = I_{max} X_L$$

$$V_{Cmax} = I_{max} X_C$$

Value at specific time (phasors)

y component gives voltage

$V_{\text{-Inductor}}$ Leads current

$V_{\text{-Capacitor}}$ Lags current

