

Calculation



Consider the harmonically driven series *LCR* circuit shown.

$$V_{max} = 100 \text{ V}$$

$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V}$$

The current leads generator voltage by 45°

L and *R* are unknown.

What is X_L , the reactance of the inductor, at this frequency?


What is *Z*, the total impedance of the circuit?

A) 70.7 k Ω

B) 50 k Ω

C) 35.4 k Ω

D) 21.1 k Ω

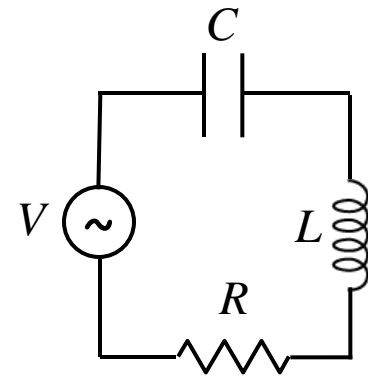

$$Z = \frac{V_{max}}{I_{max}} = \frac{100V}{2mA} = 50k\Omega$$