

Calculation



Consider the harmonically driven series *LCR* circuit shown.

$$V_{max} = 100 \text{ V}$$


$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V}$$

The current leads generator voltage by 45°

L and *R* are unknown.

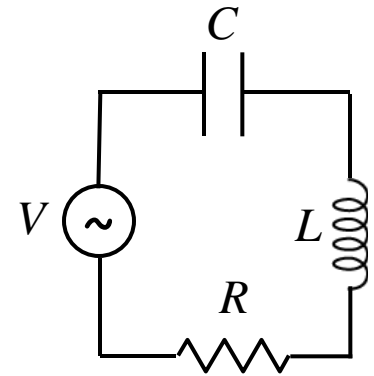What is X_L , the reactance of the inductor, at this frequency?



$$Z = 50 \text{ k}\Omega$$

$$\sin(45) = .707$$

$$\cos(45) = .707$$

What is *R*?


A) $70.7 \text{ k}\Omega$

B) $50 \text{ k}\Omega$

C) $35.4 \text{ k}\Omega$

D) $21.1 \text{ k}\Omega$

Determined from impedance triangle

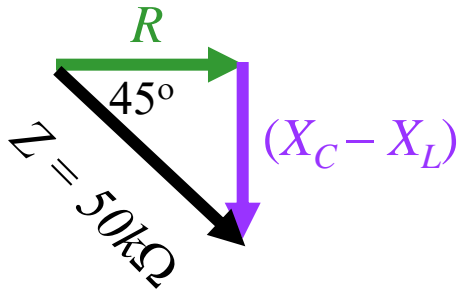

$$\cos(45) = \frac{R}{Z} \quad \rightarrow \quad R = Z \cos(45^\circ)$$
$$= 50 \text{ k}\Omega \times 0.707$$
$$= 35.4 \text{ k}\Omega$$