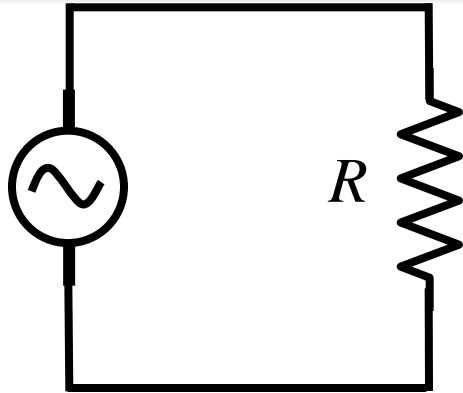



# Summary



$$I_{max} = V_{max}/R$$

$V_R$  in phase with  $I$

Because resistors are simple

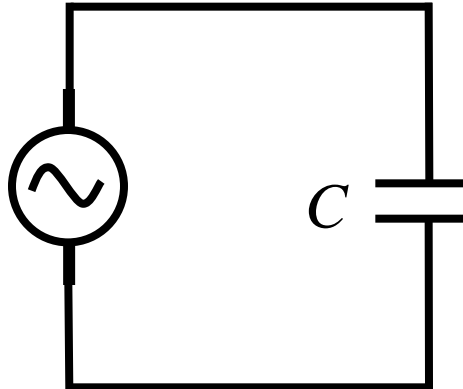


$$I_{max} = V_{max}/X_C$$

$$X_C = 1/\omega C$$

$V_C$   $90^\circ$  behind  $I$

Current comes first since it charges capacitor

Like a wire at high  $\omega$

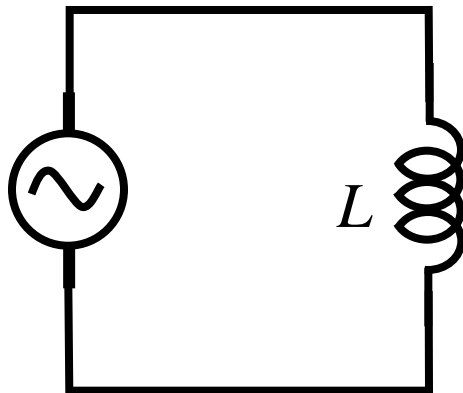

$$I_{max} = V_{max}/X_L$$

$$X_L = \omega L$$

$V_L$   $90^\circ$  ahead of  $I$

Opposite of capacitor

Like a wire at low  $\omega$